

Note – Answer all Questions.

I Discuss two port Devices and the H-parameters. Give a detailed ac Analysis on Small- Signal Low-Frequency Common-Emitter Transistor Amplifier. (12)

II (a) Explain Tunnel Diode and its characteristic. (6x2)

(b) If resistivity of pure Silicon is  $3000\Omega\text{m}$  and the electron and hole motilities are  $0.12\text{m}^2\text{v}^{-1}\text{s}^{-1}$  and  $0.045\text{m}^2\text{v}^{-1}\text{s}^{-1}$  respectively, determine. The resistivity of a specimen of the material when  $10^{19}$  atoms of phosphorous are added per  $\text{m}^3$  given  $e=1.6\times 10^{-19}\text{C}$ ,  $\rho=3000\Omega\text{m}$ ,  $\mu_e=0.12\text{m}^2\text{v}^{-1}\text{s}^{-1}$ ,  $\mu_h=0.045\text{m}^2\text{v}^{-1}\text{s}^{-1}$ .

III (a) A voltage of  $200 \cos \omega t$  is applied to Half Wave Rectifier with load resistance of  $5 \text{ kW}$ ,: (6x2)  
Find the followings

(i) Maximum DC Current Component, (ii) RMS Current, (iii) Ripple Factor (iv) TUF (v) Rectifier Efficiency.

(b) Discuss clipping circuits. Do mention the differences between inductive and capacitive filter.

IV (a) For the emitter stabilised biased circuit given in Figure-1, Determine the following (7x2)

(i)  $I_{BQ}$  (ii)  $I_{CQ}$  (iii)  $V_{CEQ}$  (iv)  $V_C$  (v)  $V_B$  (vi)  $V_E$

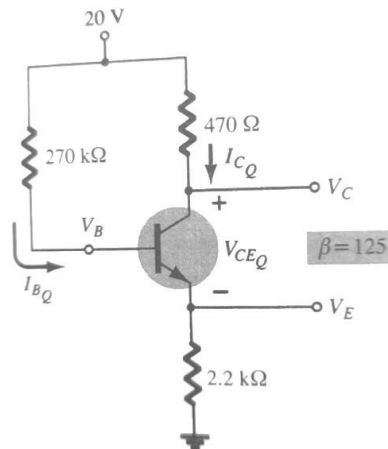


Figure-1

(b) Determine the following for the network given in Figure-2

(i)  $S(I_{CO})$  (ii)  $S(V_{BE})$  (iii) Determine the net change in  $I_C$  if a change in operating conditions results in  $I_{CO}$  increasing from 0.2 micro-ampere,  $V_{BE}$  drops from 0.7 V to 0.5 V, and  $\beta$  increases 25%.

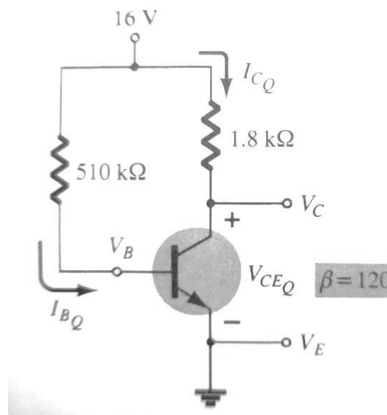


Figure 2

03/12/17  
(E)

B-2 and B-3  
IIT, Una

Dr. Shweta Chauhan  
179

Name:

Roll No:

**National Institute of Technology Hamirpur (HP)**

**Name of Examination: End-Semester Examination, B.Tech- Nov. / Dec., 2017**

Branch : Electronics & Communication Engineering.

Course Name : Basic Electronics Engineering

Semester : 1<sup>st</sup>

Course Code : ECD-114

Time : 3 Hours

Max Marks : 60

- Note: 1. All questions are compulsory.  
2. Symbols are having usual meanings.  
3. Assume necessary data if necessary.



Q.1 (a) Explain the working of Photodiode. (2)

(b) A half wave rectifier uses a diode with an equivalent forward resistance of  $0.3 \Omega$ . If the input voltage is 10V(rms) and the load is a resistance of  $2.0 \Omega$ , calculate  $I_{dc}$  and  $I_{rms}$  in the load. (2)

(c) What is the concentration of holes in Si crystals having donor concentration of  $1.4 \times 10^{24} / \text{cm}^3$  when the intrinsic carrier concentration is  $1.4 \times 10^{18} / \text{cm}^3$ ? Find the ratio of electron to hole concentration. (2)

(d) The intrinsic carrier concentration for silicon at room temperature is  $1.5 \times 10^{10} / \text{cm}^3$ . If the mobilities of electron and holes are  $1,300 \text{ cm}^2/\text{Vs}$  and  $450 \text{ cm}^2/\text{Vs}$  respectively, what is the conductivity of the silicon (intrinsic)? if silicon is doped with  $10^{18}$  boron atoms per cc, what is its conductivity? (2)

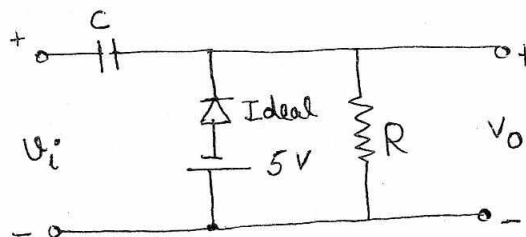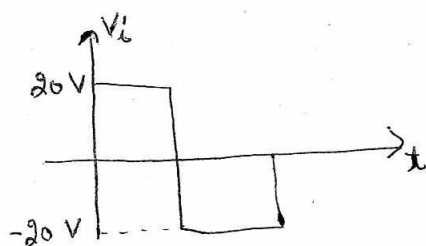(e) Determine the output waveform for the circuit shown below (2)



Q.2 (a) What are the Barkhausen conditions of oscillations in electronic systems? What are their significance? (4)

(b) Draw the circuit diagram of a two stage RC coupled amplifier using transistor and also explain the advantage, disadvantage and frequency response of RC coupled amplifier. Why we prefer decibel scale to express the gain of an amplifier? (6)

Q.3 (a) Explain the merits and demerits of negative feedback in amplifier? (5)

(b) Explain the construction, working, characteristics and parameters of N-channel JFET. (5)

(d) State and Explain the hybrid equivalent circuit of a CE transistor and also derive current gain, voltage gain, input resistance and power gain in CE transistor amplifier using h-parameters. (5)

(e) Explain FIXED BIAS CIRCUIT. In spite of its simplicity, is not much used in amplifiers. why ? (5)

Q.4 (a) Explain the difference between avalanche and zener breakdown. (2)


(b) How zener diode can be used as voltage regulator? (4)

(d) Explain the thermal runaway in transistor? (2)

(e) Difference between BJT and FET (2)


Q.6 (a) Write all the characteristics of ideal operational amplifier. (2)

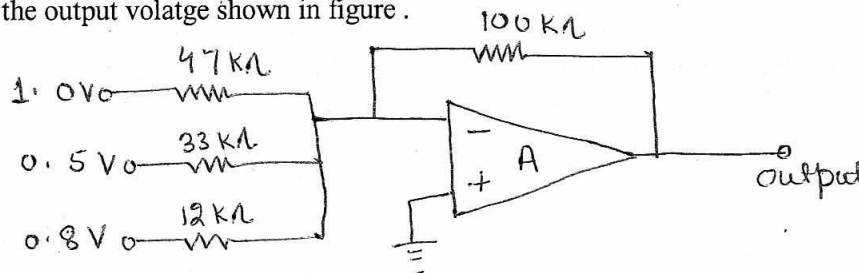(b) Determine the output voltage shown in figure. (2)




(c) Derive equation  $I_C = \beta I_B + (\beta + 1) I_{CO}$ . Explain different terms used in them. (2)

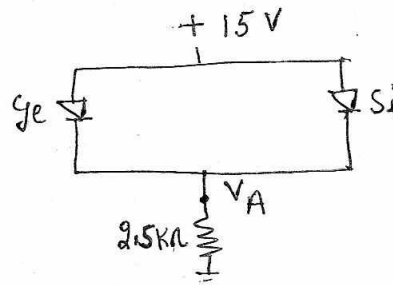(d) Determine the voltage shown in  $V_A$  shown in figure (2)




(e) Find the operating frequency of a transistor Colpitt's oscillator if  $C_1 = 30\text{pF}$ ,  $C_2 = 60\text{pF}$  and  $L = 10\mu\text{H}$ . (2)

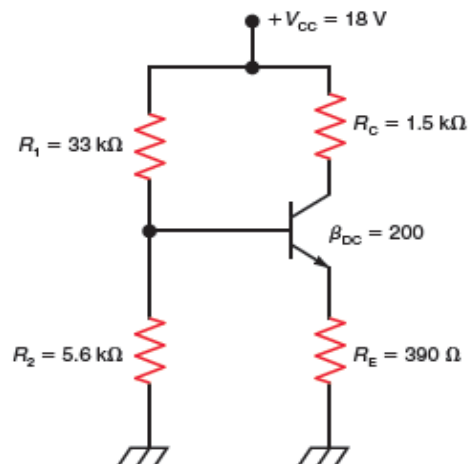
1. For the following transistor bias circuit find the  $V_B$ ,  $V_C$ ,  $V_E$ ,  $I_C$  and  $V_{CE}$ . Further also find  $I_{C(sat)}$  and  $V_{CE(off)}$ . Finally, construct a DC load line showing the coordinates of Q point and end of the load lines. (7)



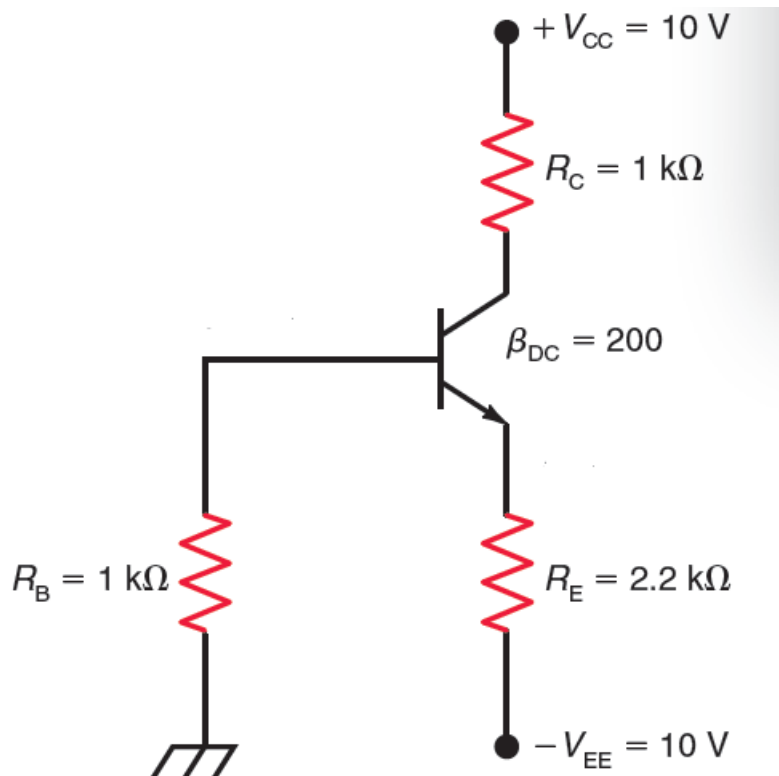
2. For the following circuit find the values of  $I_E$  and  $V_C$ . (6)



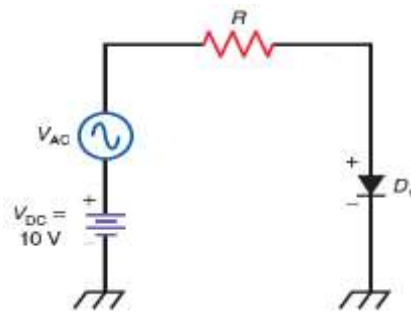
3. For the following circuit calculate the AC resistance,  $r_{AC}$ , of the diode for the following values of  $R$ :  
(a)  $10\text{ k}\Omega$  (b)  $5\text{ k}\Omega$ , and (c)  $1\text{ k}\Omega$ . (6)



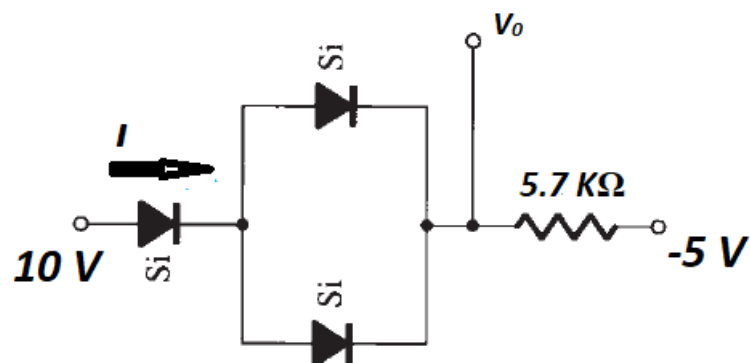4. Determine the voltage  $V_o$  and current  $I$  marked in the following figure. (4)



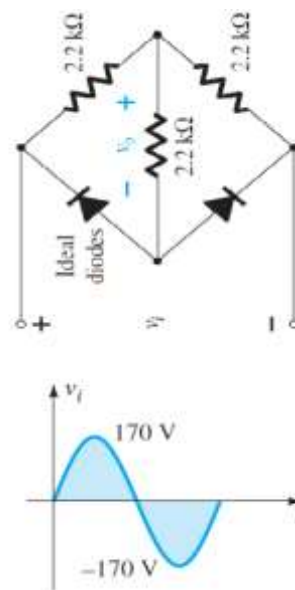6. Draw the equivalent circuits for positive and negative half cycles of the input voltage. Further draw the output voltage waveform  $v_o$  and determine the average output voltage. (6)



7. Draw hybrid equivalent model of BJT. Further for fixed bias configuration of the BJT, derive the expressions for input impedance, output impedance, voltage gain, and current gain. (7)

8. With clear diagrams explain the characteristics a junction field effect transistor. **(4)**
9. With a valid diagram discuss different current components of a BJT. **(4)**
10. With valid diagrams explain the BJT common emitter input and output characteristics. **(6)**